

A. 209_{dec} to binary

$$\begin{array}{rcl}
 209/2 & = & 104 \text{ r } 1 \\
 104/2 & = & 52 \text{ r } 0 \\
 52/2 & = & 26 \text{ r } 0 \\
 26/2 & = & 13 \text{ r } 0 \\
 13/2 & = & 6 \text{ r } 1 \\
 6/2 & = & 3 \text{ r } 0 \\
 3/2 & = & 1 \text{ r } 1 \\
 1/2 & = & 0 \text{ r } 1
 \end{array}$$

$$209_{10} = 11010001_2$$

$$\underline{1101 \quad 0001}$$

B. -117 in signed magnitude

first bit is 1 because negative

$$\begin{array}{rcl}
 117/2 & = & 58 \text{ r } 1 \\
 58/2 & = & 29 \text{ r } 0 \\
 29/2 & = & 14 \text{ r } 1 \\
 14/2 & = & 7 \text{ r } 0 \\
 7/2 & = & 3 \text{ r } 1 \\
 3/2 & = & 1 \text{ r } 1 \\
 1/2 & = & 0 \text{ r } 1
 \end{array}$$

1110101, in signed magnitude is

$$\underline{1111 \quad 0101}$$

C. -117 in two complement

117 in 8 bits is 0111 0101

$$\begin{array}{r} \text{bits slipped} \quad 1000 \quad 1010 \\ + 0000 \quad 0001 \\ \hline \end{array}$$

$$1000 \quad 1011$$

$$\underline{1000 \quad 1011}$$

D 4.75

4 in 4bit binary = 0100

$$\begin{array}{cccc} 2^{-1} & 2^{-2} & 2^{-3} & 2^{-4} \\ 0.5 & 0.25 & 0 & 0 \\ \hline \end{array}$$

$$0.75 = 1100$$

therefore 4.75 = 0100 1100

E. Fish in ascii

F = 01000110 Parity bit
odd 1

i = 01101001 even 0

s = 01110011 odd 1

h = 01101000 odd 1

F i s h

1100 0110 0110 1001 1011 0011 1110 1000

F. F7 in binary

F in binary is 1111 (15)

7 in binary is 0111
2² 2¹ 2⁰

4 + 2 + 1

F7 = 1111 0111

G) 123_8 to base 2

A

$$\begin{array}{l} 1 = 001 \\ 2 = 010 \\ 3 = 011 \end{array}$$

combined this gives us 001010011

as this is 9 digits we can remove
a leading 0 to give us

01010011
or 0101 0011

Question 2

A) Truth table

M	N	O	BUY
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

B) KMap


M \ NO	NO			
	00	01	11	10
00	0	1	1	0
01	0	1	1	1

C) Simplify Expression


The first group is O, the second group is M and N.

Therefore our simplified expression is $O + MN$


D) Implement circuit diagram

 

E) Reimplement with only NOR gates

 

3

 

Clock	R	S	Q
0	-	-	Previous
1	0	0	Previous
1	0	0 1	1
1	0 1	0	0
1	1	1	Wont work

3) Part 2

A clocked SR flip flop will only update its output when the clock signal is set to 1, this is because the first set of NAND gates will always output a 1 unless both inputs are a 1. By setting S to 1 and Clock to 1, Q is set to 1. By setting R to 1 and clock to 1, Q is reset to 0.

4

part 1


x	y	z	parity
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

x \ yz	00	01	10	11
0	0	1	1	0
1	1	0	0	1

cant be simplified

therefore

$$xy'z' + x'y'z + xyz + x'yz'$$

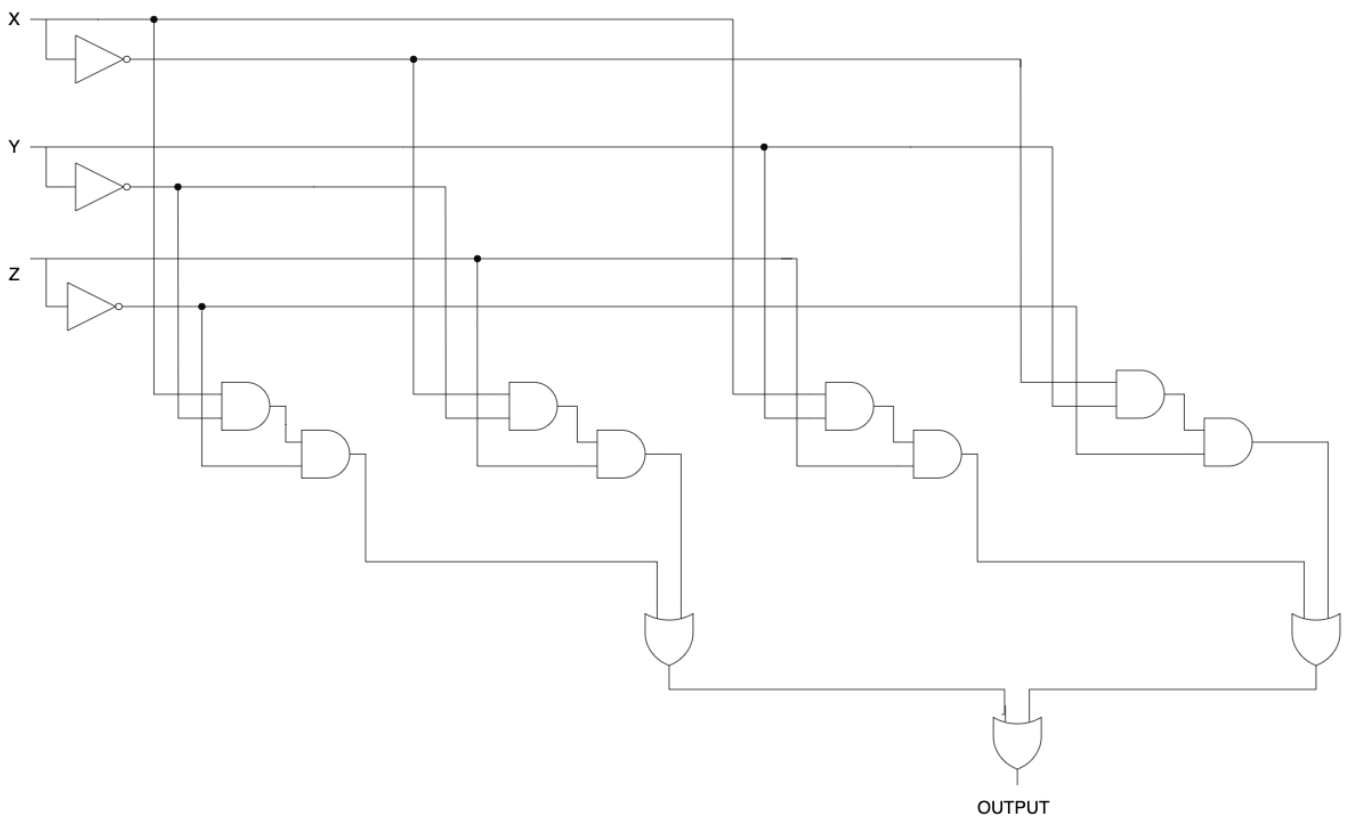

The parity bit generator table given is for an even parity bit system, this means if there is an odd number of 1s in a sequence then the parity bit must also be a 1. The circuit above does this by giving each input two outputs, its regular output and its complement. These are then fed into a series of AND gates which check how many 1s are in the input.

The first three sets of AND gates check that there is only one 1 in the sequence, the final set of and gates check to see if there are three 1s. Finally each of these sets of and gates are combined with multiple OR gates.